

Want about voltage at 2.8 kHz from the -ve to +ve SPL

↳ difficult to get without full data sheet but can estimate it to be in micro volt

↳ we want to adjust everything to precision

Need to flow of circuit to build:

NIC-E1 PCB → coupling + bias → pre-Amp

Comparator ← Envelope detector
Feedback

Bias Resistor

→ provide DC voltage to power internal FET
→ limit current to safe levels

$$R_B = \frac{V_{mic_supply} - V_{mic_operating}}{I_{max}}$$


Using 5V supply where the comparitor will be the buffer to supply 3.3V to the ES932 to start to damage.

- $R_B = \frac{5 - V_{mic_operating}}{0.5 \times 10^{-3}}$ → $V_{mic_operating}$ is not enough will need a 10k resistor as per max is 10 kΩ well. to ensure 0.5 mA range is 0 - 10 kΩ.

$$f_c = \frac{1}{2\pi \cdot R_{load} \cdot C_{coupling}}$$

Currently we have:

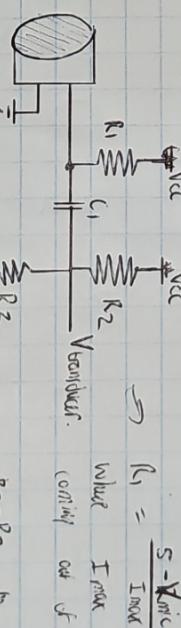AC signal from microphone → this needs to be bridged to supply about 0 - 5V



$$R_1 = \frac{5 - V_{mic}}{I_{max}}$$

where I_{max} is the max current coming out of transducer.

$R_2 = R_1$ to make a 2.5V bias by sum of the AC signal from the transducer.

This voltage is then fed into L-Tspice will be used to simulate this design to ensure full operation.

Adding a source of 25 mV to simulate the voltage from the microphone.

Resolution of normal voltage source is too low → makes a jumpy wave not smooth at a specific frequency.

- Need to add: options divide = 21, ref10 = 1u, v101 = 1n.
↳ Fixed issue.

New oscillates about 2.5V with min volts at the input.

08/08/2025

08/08/2025